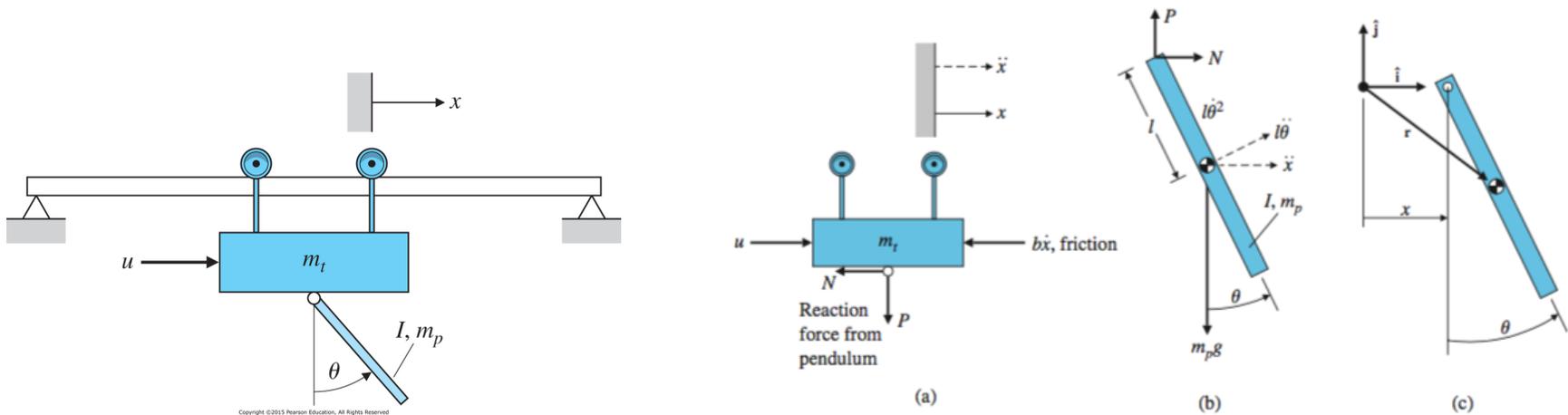


3. Combined Rotation and Translation

- The procedures to obtain the equation of motion are listed:
 - (1) sketch the free-body diagrams
 - (2) define coordinates and positive directions
 - (3) determine all forces and moments acting
 - (4) apply Newton's law and Euler's law
 - (5) combine the equations to eliminate internal forces
 - (6) check whether or not the number of independent equations is equal to the number of unknowns.



- (Example 2.8, Hanging Crane) Assume that the moment of inertia I is denoted in terms of the mass center. For the pendulum,

$$\begin{aligned}
 N &= m_p \ddot{x} + m_p l \ddot{\theta} \cos \theta - m_p l \dot{\theta}^2 \sin \theta \\
 P - m_p g &= m_p l \ddot{\theta} \sin \theta + m_p l \dot{\theta}^2 \cos \theta \\
 -Pl \sin \theta - Nl \cos \theta &= I \ddot{\theta} \quad \rightarrow \quad (I + m_p l^2) \ddot{\theta} + m_p g l \sin \theta = -m_p \ddot{x} l \cos \theta
 \end{aligned}$$

For the crane,

$$m_t \ddot{x} = u - N - b\dot{x} \quad \rightarrow \quad (m_t + m_p)\ddot{x} + b\dot{x} + m_p l \ddot{\theta} \cos \theta - m_p l \dot{\theta}^2 \sin \theta = u$$

As a result, we have the complete equation of motion:


$$\begin{aligned} (I + m_p l^2) \ddot{\theta} + m_p g l \sin \theta + m_p \ddot{x} l \cos \theta &= 0 \\ (m_t + m_p) \ddot{x} + b\dot{x} + m_p l \ddot{\theta} \cos \theta - m_p l \dot{\theta}^2 \sin \theta &= u \end{aligned}$$

For the linearization with small angle variation, $\sin \theta \approx \theta$, $\cos \theta \approx 1$ and $\dot{\theta}^2 \approx 0$, we have

$$\begin{aligned} (I + m_p l^2) \ddot{\theta} + m_p g l \theta + m_p l \ddot{x} &= 0 \\ (m_t + m_p) \ddot{x} + b\dot{x} + m_p l \ddot{\theta} &= u \end{aligned}$$

Furthermore, ignoring the damping b , we can get the TF as follow:





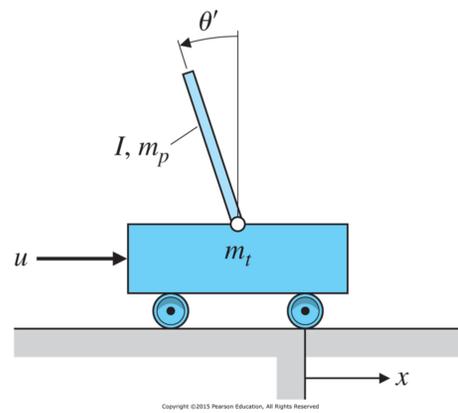
$$\frac{\Theta(s)}{U(s)} = \frac{-m_p l}{[(m_t + m_p)(I + m_p l^2) - m_p^2 l^2] s^2 + (m_t + m_p) m_p g l}$$



- (Homework #1, Due : March 29th, 2020) Derive the equation of motion (for the inverted pendulum on a cart (Segway)) as the complete version and the linearized version.?


2 Models of Electrical Circuits

1. Consider the elements of electric circuits such as resistor, capacitor, inductor, voltage source, and current source.

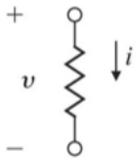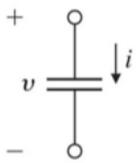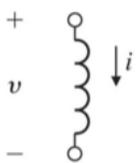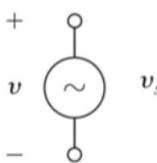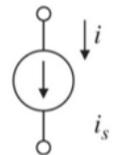	Symbol	Equation
Resistor		$v = Ri$
Capacitor		$i = C \frac{dv}{dt}$
Inductor		$v = L \frac{di}{dt}$
Voltage source		$v = v_s$
Current source		$i = i_s$

Copyright ©2015 Pearson Education, All Rights Reserved

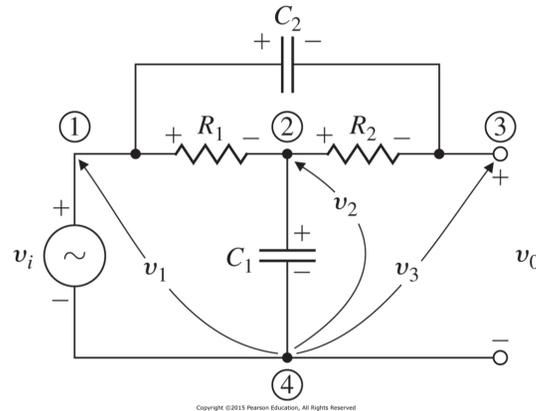2. (Kirchhoff's current law, KCL) The algebraic sum of currents leaving a junction or node equals the algebraic sum of currents entering that node.
3. (Kirchhoff's voltage law, KVL) The algebraic sum of all voltages taken around a closed path in a circuit is zero.



4. (Example 2.9, Bridged Tee Circuit) After assigning four node voltages, let us consider $v_4 = 0$ as reference voltage, then we know $v_1 = v_i$ and $v_3 = v_o$ at nodes 1 and 3, respectively, and, at nodes 2 and 3, we have


$$\frac{v_2 - v_1}{R_1} + C_1 \frac{dv_2}{dt} + \frac{v_2 - v_3}{R_2} = 0$$

$$\frac{v_3 - v_2}{R_2} + C_2 \frac{d(v_3 - v_1)}{dt} = 0$$

Let us take LT to derive TF $\frac{V_o(s)}{V_i(s)}$:

$$\left(\frac{1}{R_1} + C_1 s + \frac{1}{R_2} \right) V_2(s) = \frac{1}{R_1} V_i(s) + \frac{1}{R_2} V_o(s) \quad \rightarrow \quad (R_1 + R_2 + R_1 R_2 C_1 s) V_2(s) = R_2 V_i(s) + R_1 V_o(s)$$

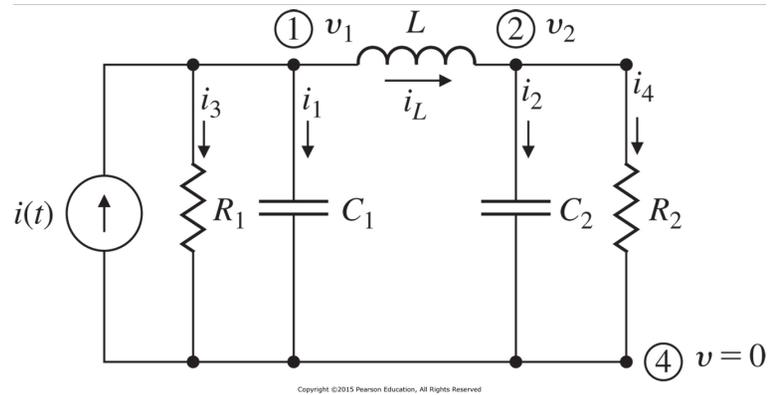
$$\left(\frac{1}{R_2} + C_2 s \right) V_o(s) = \frac{1}{R_2} V_2(s) + C_2 s V_i(s) \quad \rightarrow \quad (1 + R_2 C_2 s) V_o(s) = V_2(s) + R_2 C_2 s V_i(s)$$



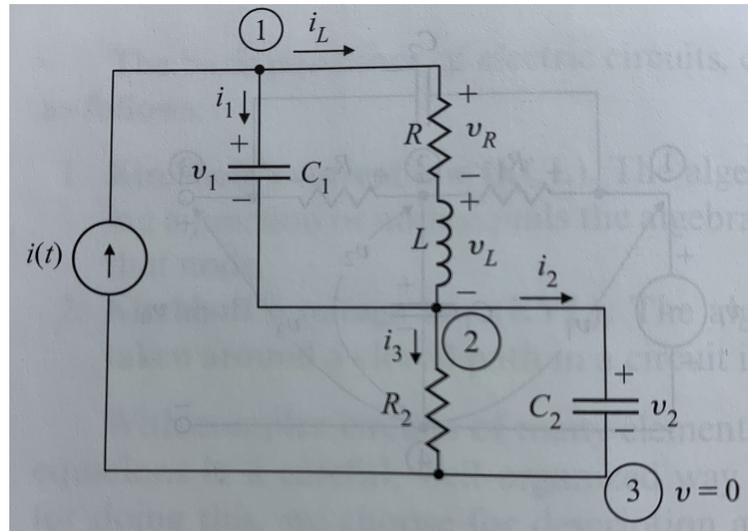5. (Example, Circuit with Current Source)

$$\begin{aligned}
 -i(t) + \frac{v_1}{R_1} + C_1 \frac{dv_1}{dt} + i_L &= 0 & \rightarrow & \quad I(s) = \left(\frac{1}{R_1} + C_1 s \right) V_1(s) + I_L(s) \\
 -i_L + C_2 \frac{dv_2}{dt} + \frac{v_2}{R_2} &= 0 & \rightarrow & \quad I_L(s) = \left(C_2 s + \frac{1}{R_2} \right) V_2(s) \\
 v_1 - v_2 &= L \frac{di_L}{dt} & \rightarrow & \quad V_1(s) - V_2(s) = Ls I_L(s)
 \end{aligned}$$

After tedious manipulations, we can derive two TF's such as $\frac{V_1(s)}{I(s)}$ and $\frac{V_2(s)}{I(s)}$




6. (Example 2.10, Circuit with Current Source)

$$C_1 \frac{dv_1}{dt} + i_L = i(t) \quad \rightarrow \quad C_1 s V_1(s) = I(s) - I_L(s)$$

$$R i_L + L \frac{di_L}{dt} = v_1 \quad \rightarrow \quad (Ls + R) I_L(s) = V_1(s)$$

$$\frac{v_2}{R_2} + C_2 \frac{dv_2}{dt} = i(t) \quad \rightarrow \quad (C_2 s + 1/R_2) V_2(s) = I(s)$$

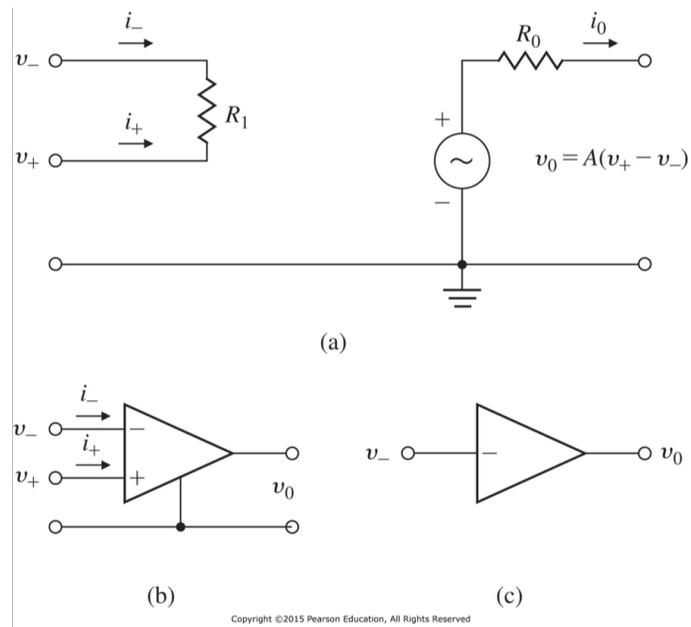After tedious manipulations, we can derive three TF's such as $\frac{V_1(s)}{I(s)}$, $\frac{V_2(s)}{I(s)}$ and $\frac{I_L(s)}{I(s)}$



7. Consider the operational amplifier (OP-amp), for a practical use in control circuits, assume that the op-amp is ideal with the


$$R_1 = \infty$$

$$R_0 = 0$$

$$A = \infty$$


$$i_+ = i_- = 0$$

$$v_+ = v_-$$

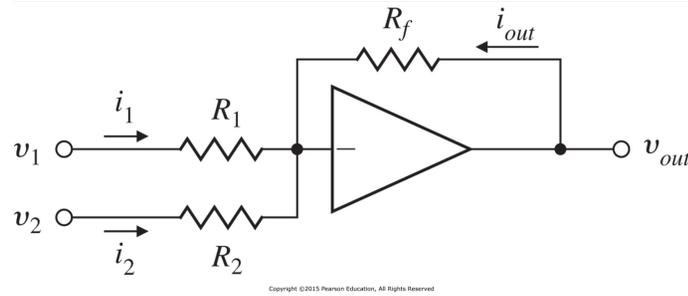

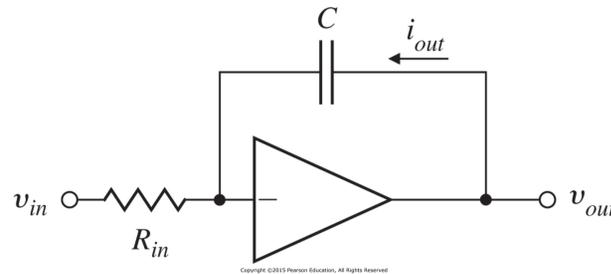8. (Example 2.11, Op-Amp Summing Circuit) weighted sum of the input voltages with a sign change.

$$\frac{0 - v_1}{R_1} + \frac{0 - v_2}{R_2} + \frac{0 - v_o}{R_f} = 0 \quad \rightarrow \quad v_o = - \left(\frac{R_f}{R_1} v_1 + \frac{R_f}{R_2} v_2 \right)$$



9. (Example 2.12, Op-Amp Integrator Circuit) integration of the input voltage with a sign change.

$$\frac{0 - v_i}{R_i} + C \frac{d(0 - v_o)}{dt} = 0 \quad \rightarrow \quad v_o(t) = -\frac{1}{R_i C} \int_0^t v_i(\tau) d\tau + v_o(0)$$

The TF with zero initial condition, we have

$$\frac{V_o(s)}{V_i(s)} = \frac{1}{R_i C s}$$